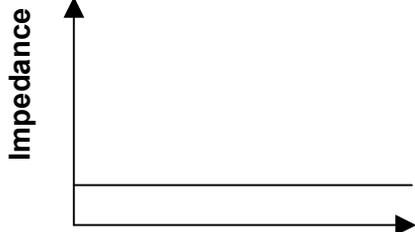
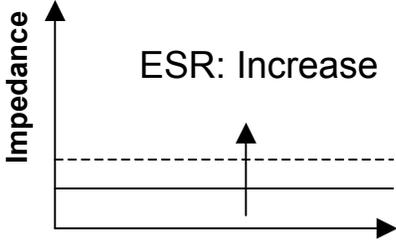
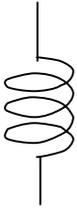
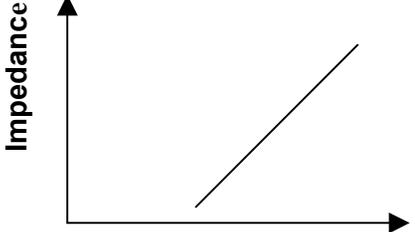
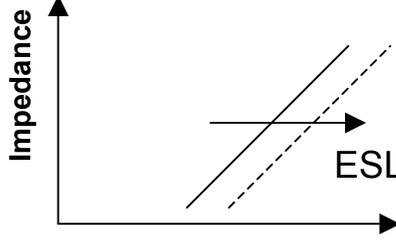
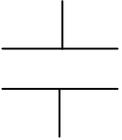
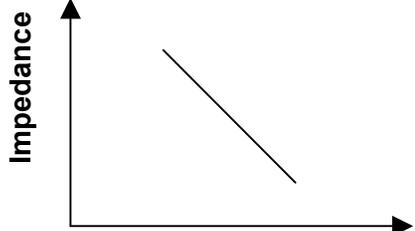
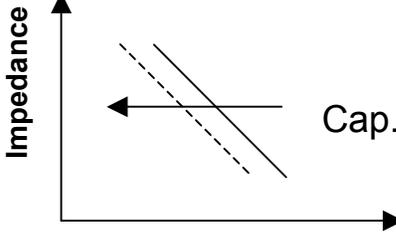


**- Chapter 1-**

# **Capacitor**

# Impedance Characteristics of Capacitor


**Impedance equivalent circuit with capacitor is the same as the RLC series model.**

| Elements in Capacitor   | Changes in Frequency   | Changes in Element  |
|---|--|---|
| <p>ESR</p>           |  <p>ESR is constant</p>        |  <p>ESR: Increase</p>    |
| <p>ESL</p>           |  <p>ESL increases</p>          |  <p>ESL: Decrease</p>    |
| <p>Capacitance</p>  |  <p>Capacitance decreases</p> |  <p>Cap. : Increase</p> |

**What happens to the impedance level when connected in series?**


# Impedance Characteristics of Capacitor

## Impedance for series connection

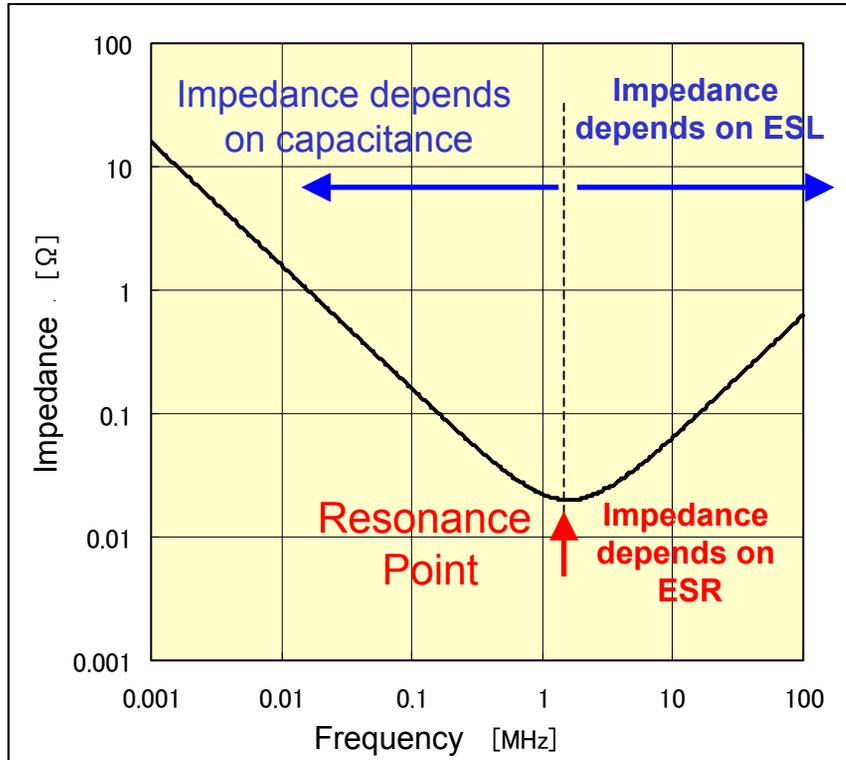

- At resonance point, no impedance for Capacitor & ESL (Impedance for ESR only)
- The frequency at resonance point depends on Capacitor & ESL

## Impedance with different elements

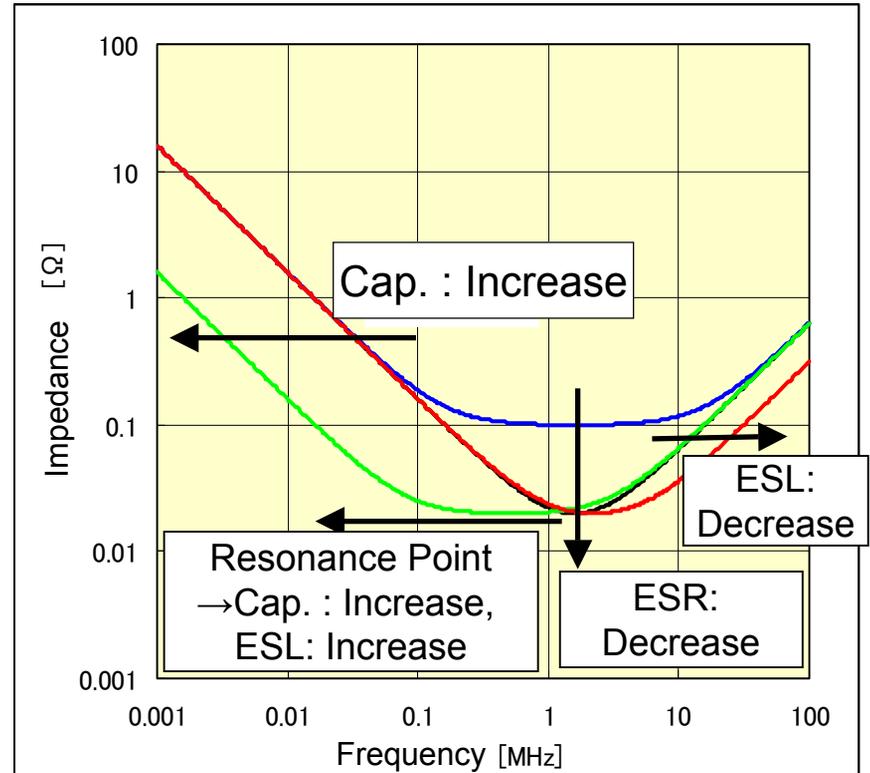


Impedance characteristics vary depended on each element.



# Reliabilities of Multi-Layered Ceramic Capacitor

## 1. Operational condition comparison chart for Circuit

|                             | Polarity  | De-rating   | Ripple CU. Limitation   | Heat Resistance  | Solvent Resistance                                    | Loading Test  |
|-----------------------------|---|---|---|--|---|---|
| MLCC                        | No  | ◎   | ◎   | ◎  | ◎   | ◎   |
| Ta Cap.                     | Yes   | ×   | △   | ×  | △   | ×   |
| Al Cap.                     | Yes   | ×   | ×   | △  | ×   | △   |
| <b>Application Problems</b> | *Layout<br>*Polarity exam When mounting<br>*Reverse voltage Consideration | *Operational limitation for rated voltage (70~50%level) | *Have margin capacity for ripple current<br>*Less reliable associated from self heating | *Limitation for reflow molding and degrading advancement | *Liquid solution flooding except block structure MLCC | *Al capacitor: decreasing in capacitance from electrolysis loss<br>*Ta capacitor: diffusion of Ag, short circuit from degrading of insulating layer |

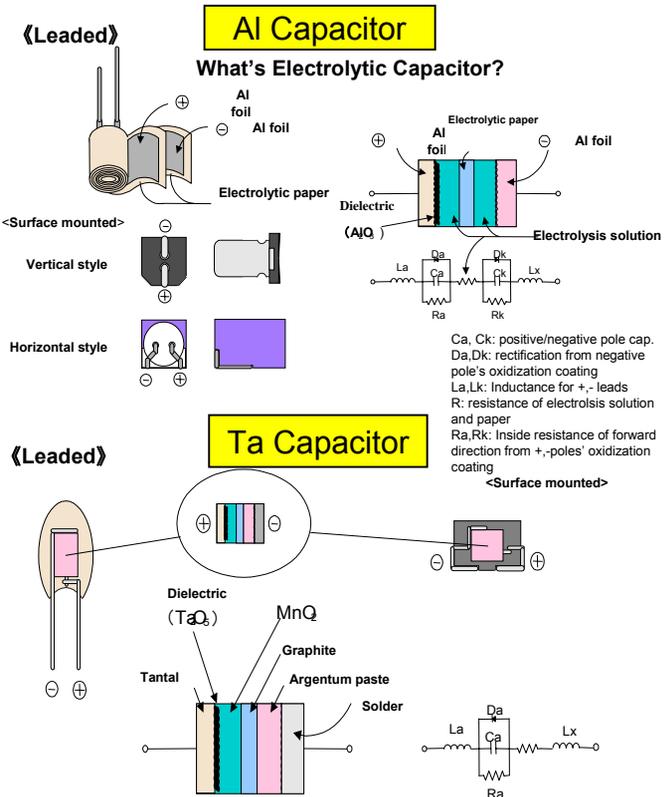


## Ceramic Capacitor

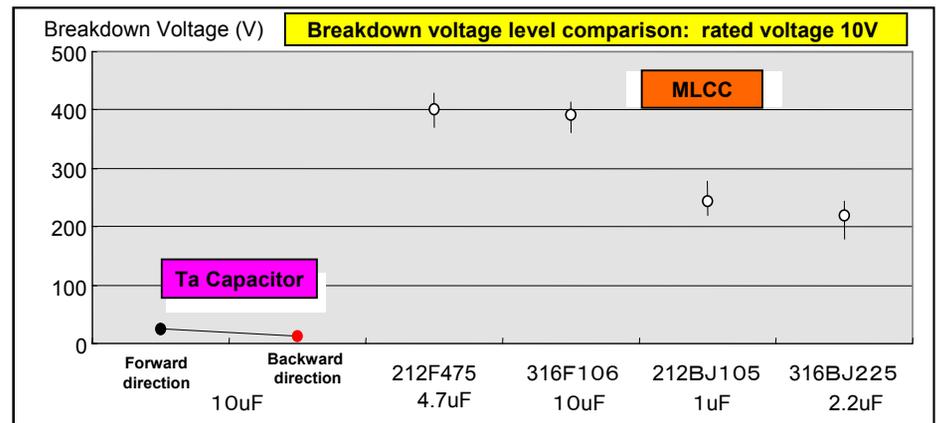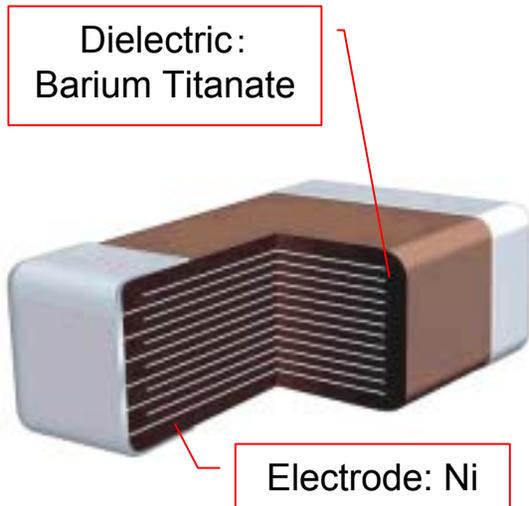


# Characteristics Comparison for the Different Type of Capacitors

## Ripple Current Characteristics

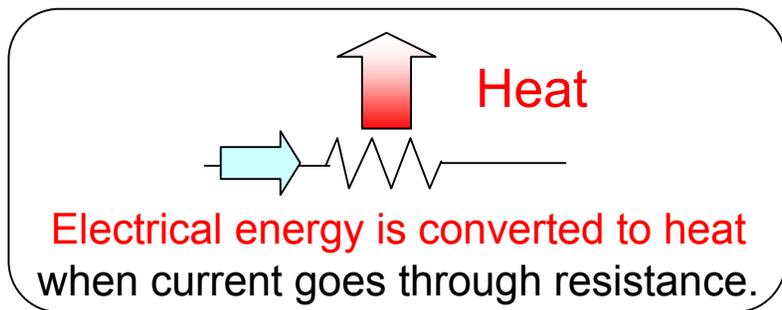


## Capacitor

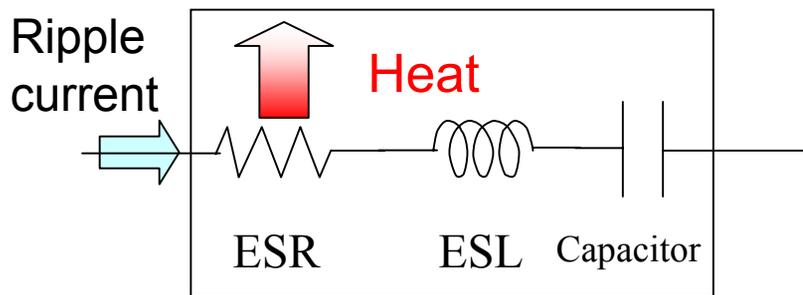

Electrical energy is converted to **heat** when **ripple current** (AC) goes through capacitor. (DC does not go through it)

**Heat** shortens capacitor's durability.
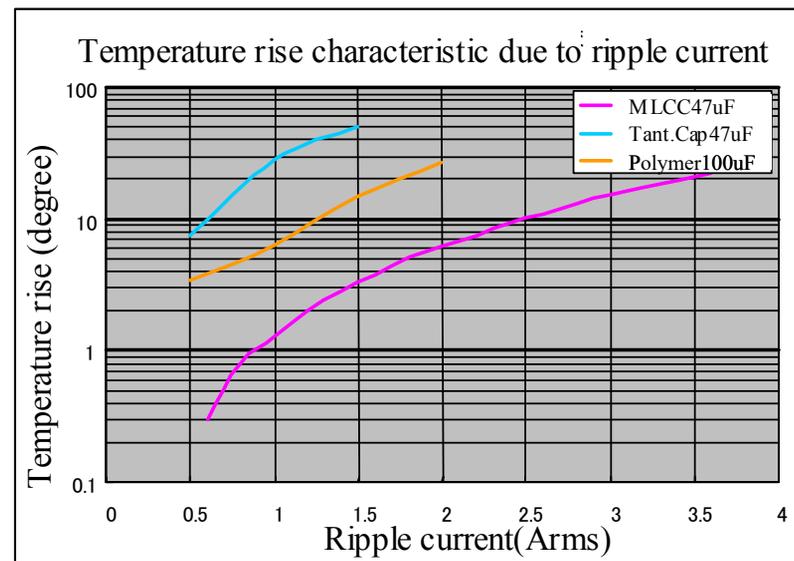
## Ripple current characteristics for the different type of capacitors



Given the same amount of calorific power, **ripple current** goes through **MLCC** the most because of its **low ESR**.

Operational recommendation of **heat release value** for MLCC is **within 10°C**.


There is no limitation of allowed ripple current for MLCC.

Operational recommendation of **heat release value** for **electrolytic capacitor** is **within 5°C**. Allowed ripple current is regulated by makers.

# **The Basic Knowledge of Circuits**

# The Functions of Bypass (decoupling) Capacitor

## The Role of Bypass Capacitor

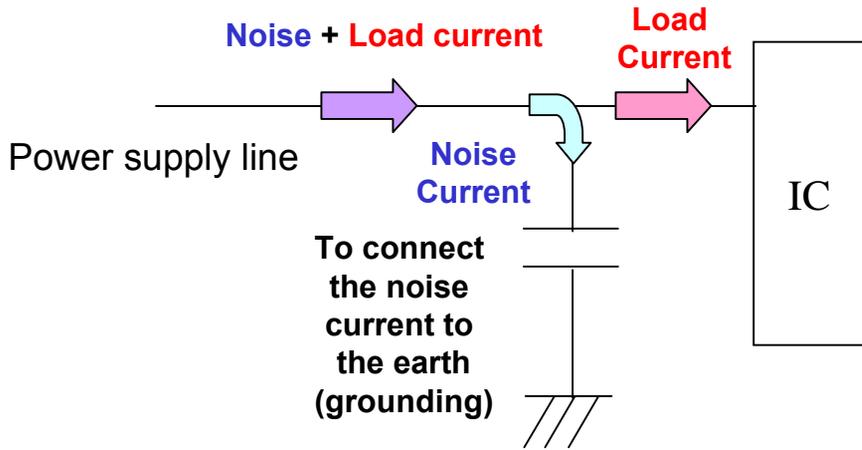


## The principle of operation for Bypass Capacitor

DC does not go through the capacitor  
(Impedance:  $\infty$ )

➡ DC is supplied directly to IC

AC (noise) does go through the capacitor

➡ AC (noise) is grounded

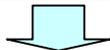


Noise Suppression → Stabilize IC operation

## Necessary Characteristics for Bypass Capacitor

It has low impedance.

(low prevention of an electric current)

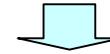


It electrifies an electric current well.



It efficiently grounds the noise current.



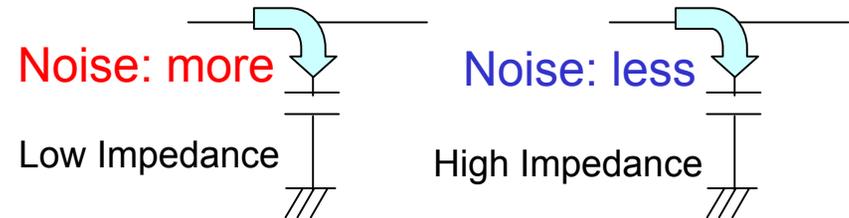
It effectively decreases the noise current.



|                            |                |   |                |
|----------------------------|----------------|---|----------------|
| Impedance                  | Low            | ↔ | High           |
| Noise effect of decreasing | More effective | ↔ | Less effective |

# The Functions of Bypass (decoupling) Capacitor

## Selection Criteria for Capacitor

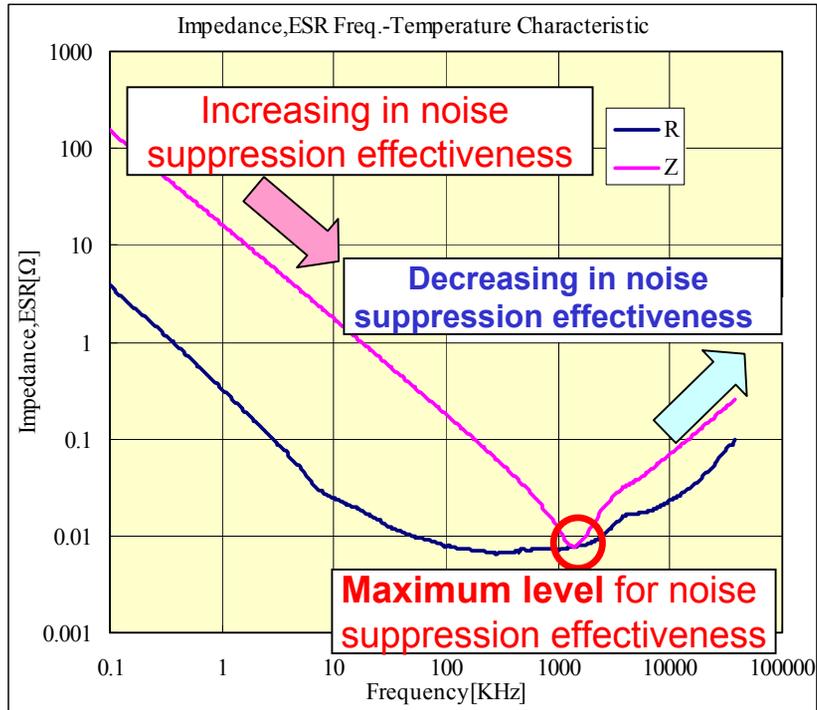

Several kinds of Noise Frequencies




Select a Capacitor based on noise frequency needs to be eliminated

# The Functions of Backup Capacitor

## Load current to IC



Load current doesn't stay constant.

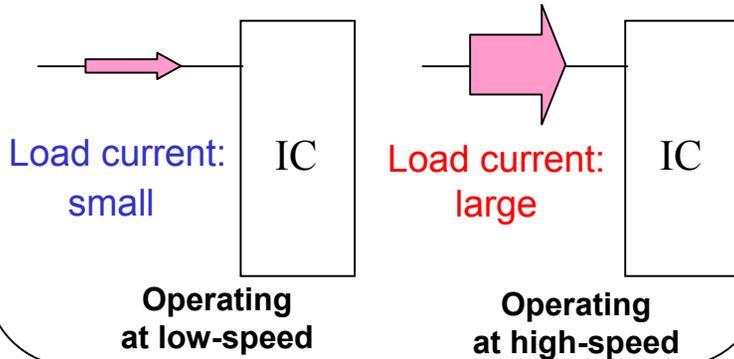

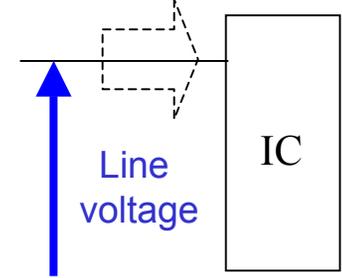
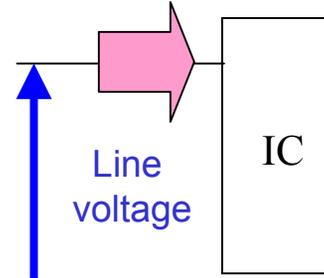
## Power line for high-speed load changing

Large load current is quickly needed.

The current can't flow to IC quickly enough.




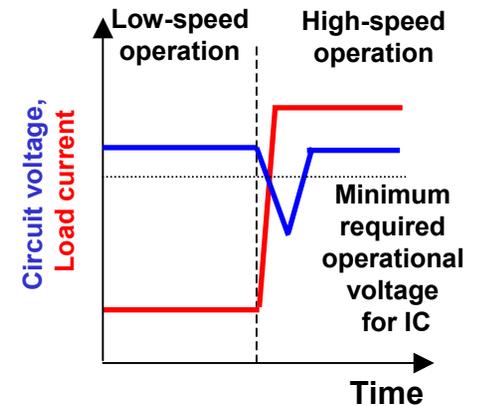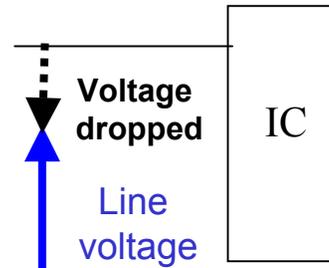Line voltage can't be maintained, therefore voltage is dropped.


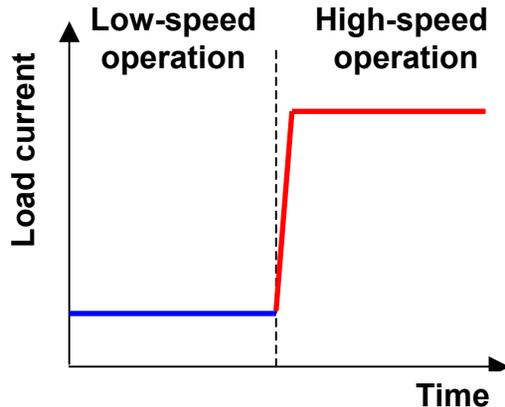
## High-speed load change

When IC's operational speed changes rapidly, large load current is quickly needed.







Line voltage decreases below the required operational voltage for IC.

The IC stops its operation.

# The Functions of Backup Capacitor


## The Role of Backup Capacitor

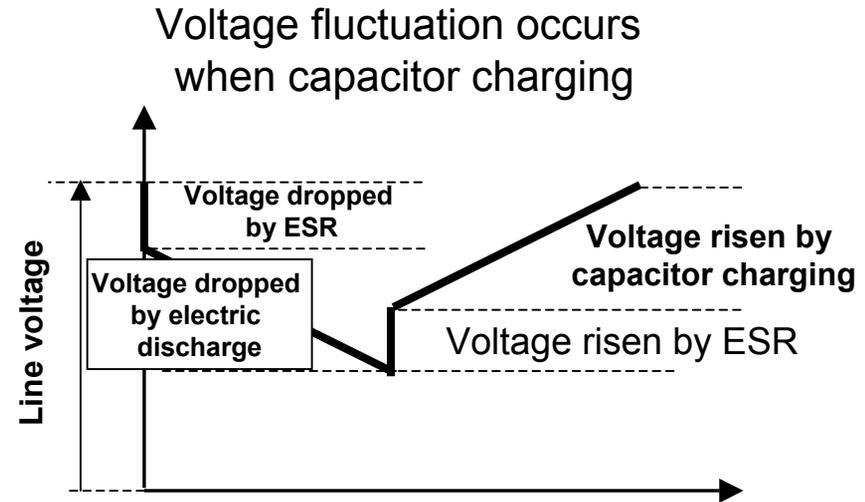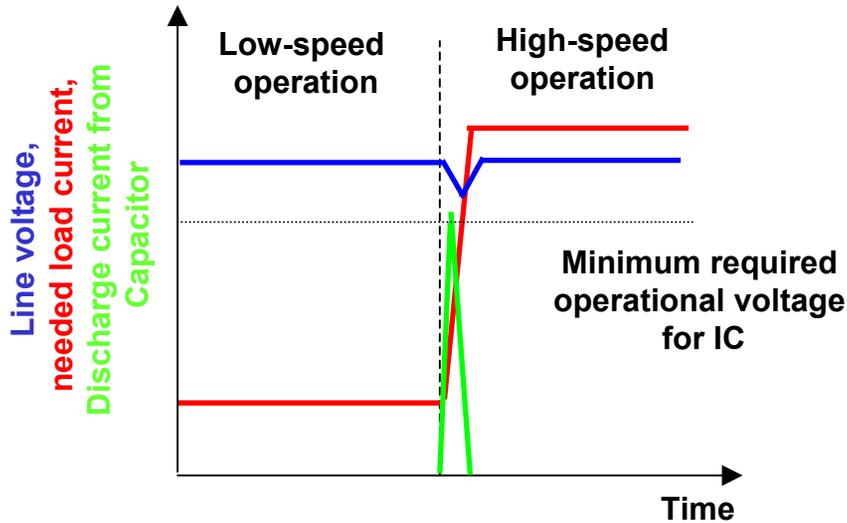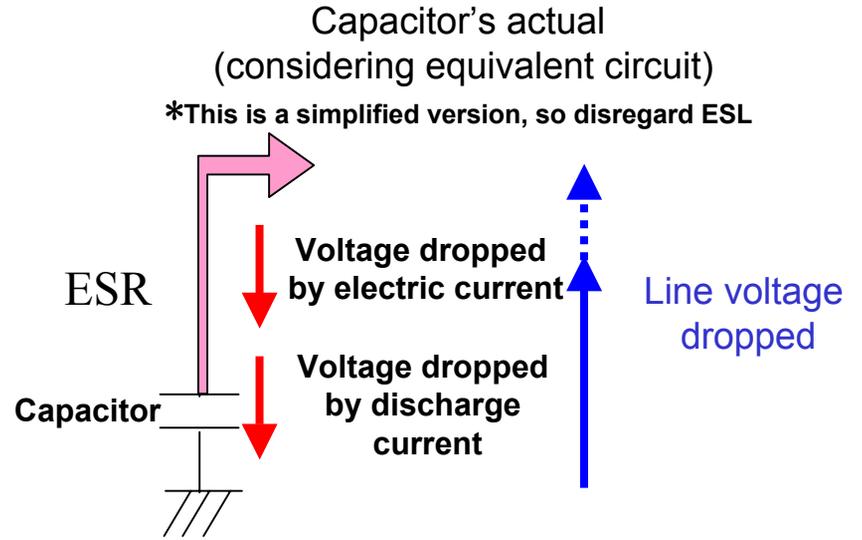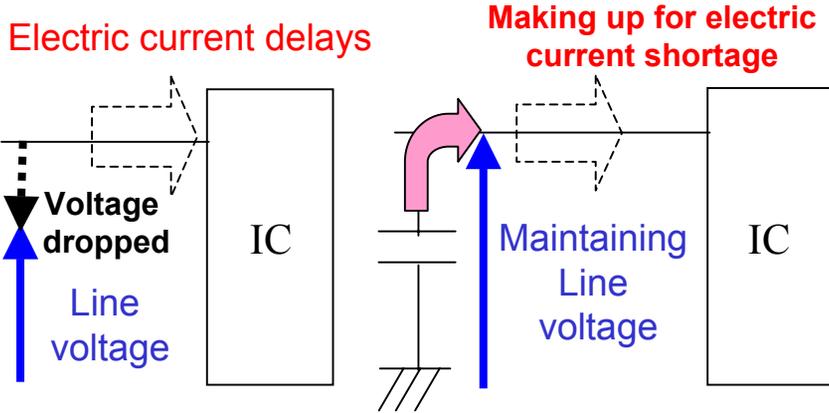


Keeping the minimum required operational voltage for IC  $\Rightarrow$  Maintaining stable operation

Capacitor and ESR decide the amount of voltage dropped


# The Functions of Backup Capacitor

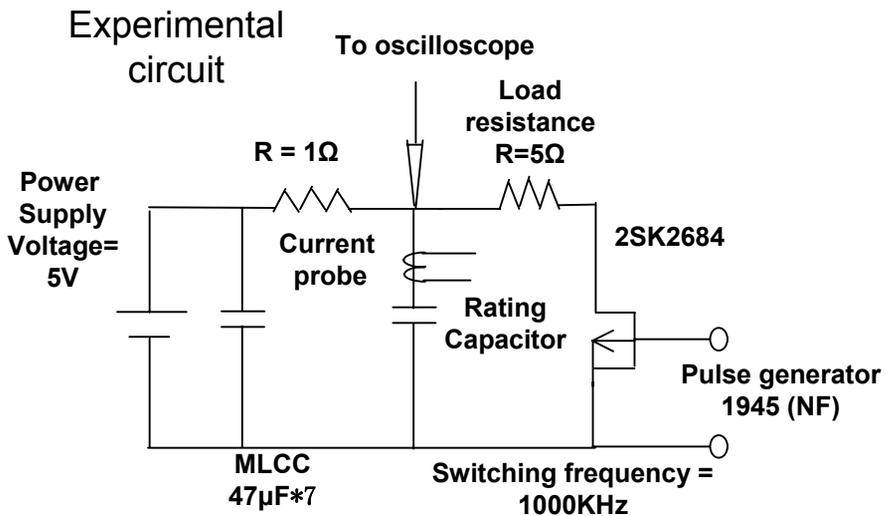

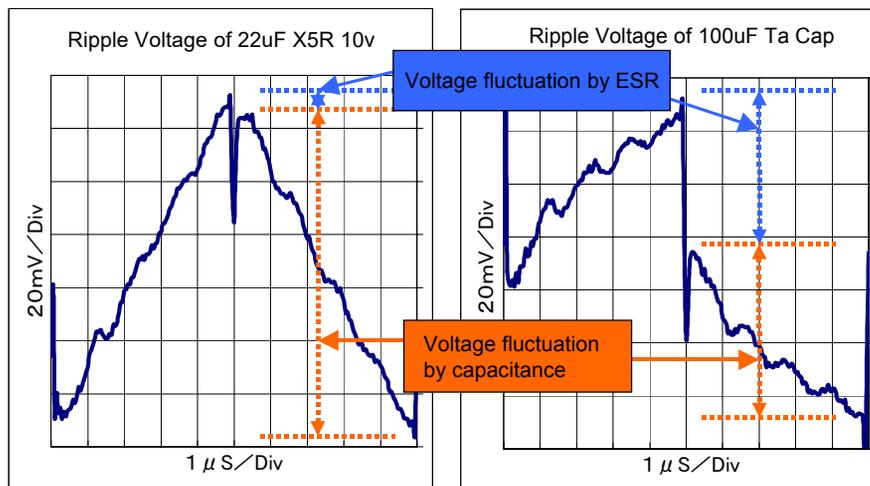
## Experimental result for Capacitance and ESR



## ESR comparison

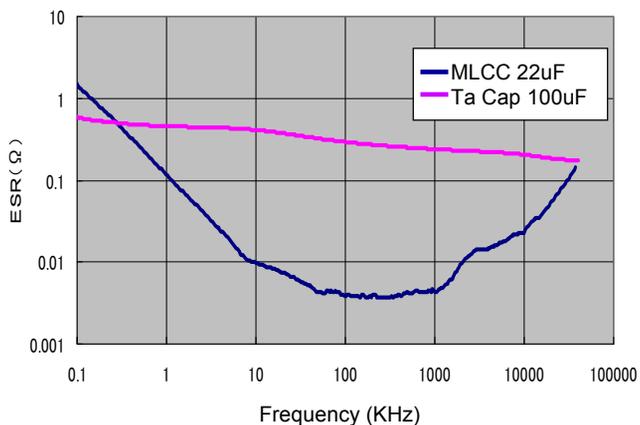

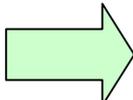High Value  
Low ESR  The fluctuation band of line becomes narrower.

## Merits of MLCC


It enables to replace Ta capacitor with a smaller value of MLCC.

The effectiveness of MLCC's voltage fluctuation depressing effect is greater than that of Ta capacitor.


# **The Basic Knowledge of Power Supply Circuit**

# Series Regulator (3 Terminal Regulator)

Circuit operation (water gate model)

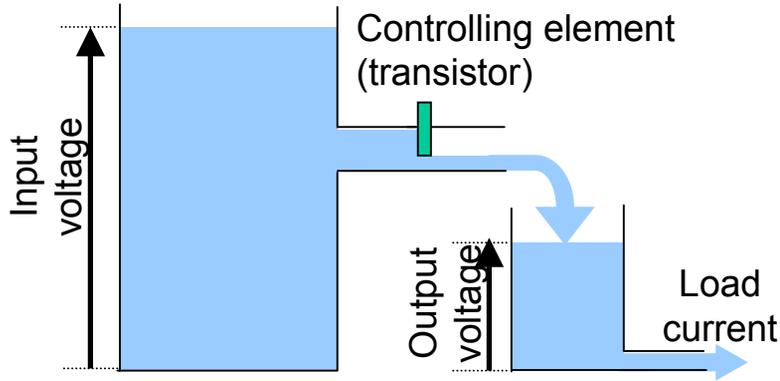


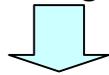Producing output voltage by lowering certain amount of input voltage



Step-down power supply

Load current fluctuation

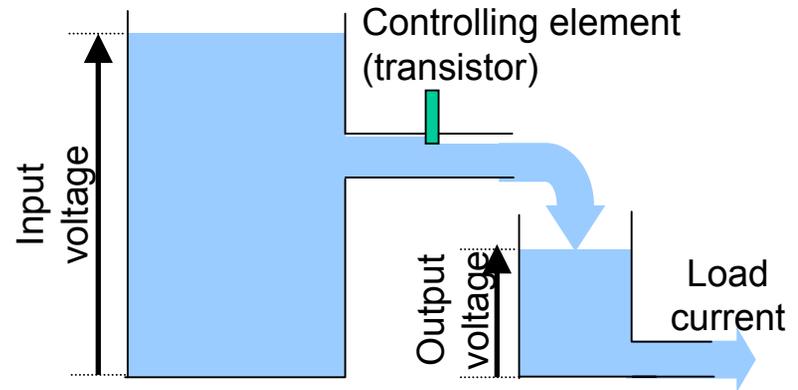

Controlling water gate to keep the water level constant


Controlling load current with transistor



**Output voltage stays constant.**

# Series Regulator (3 Terminal Regulator)

Circuit structure

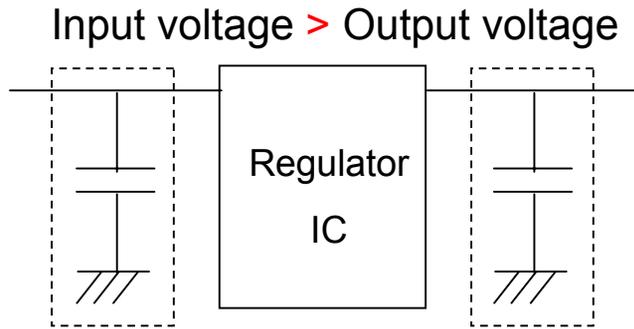


Input Capacitor

Output Capacitor


Consisting of IC, input and output capacitors.

Effects of input capacitor

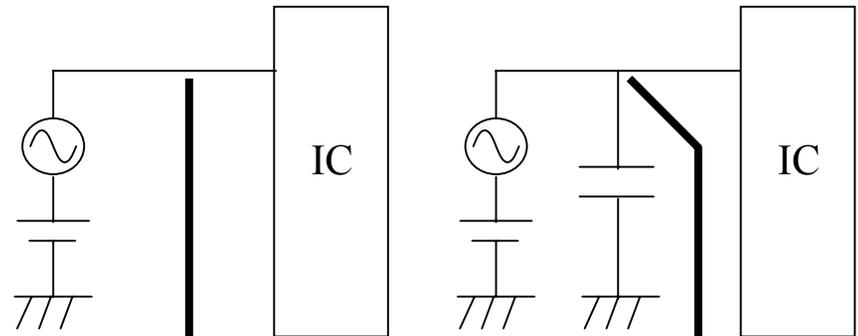
Add alternate current to input voltage purposely to measure input current amount with or without input capacitor



Function of input capacitor

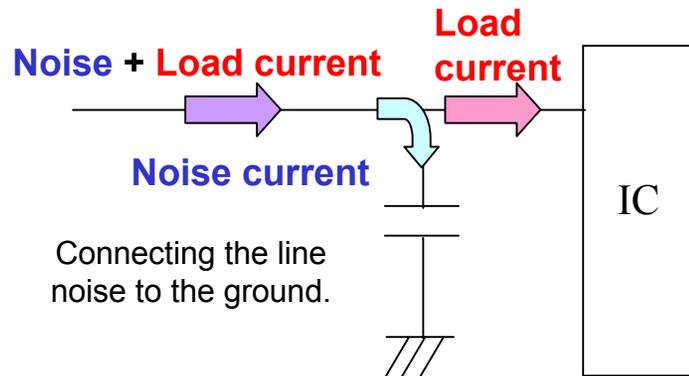

Same as the function of Bypass Capacitor

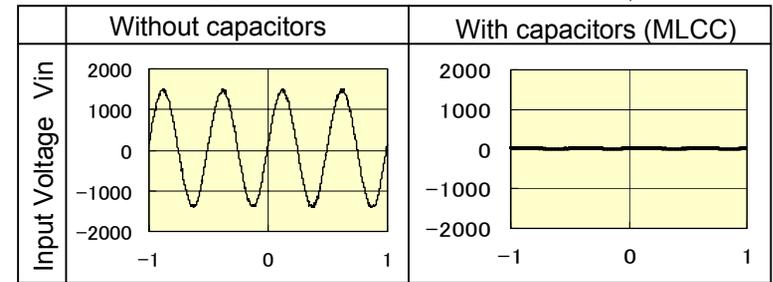


Vertical: mV Horizontal: u sec

Input voltage is stabilized as input capacitor is connected.




# Series Regulator (3 Terminal Regulator)

Function of output capacitor

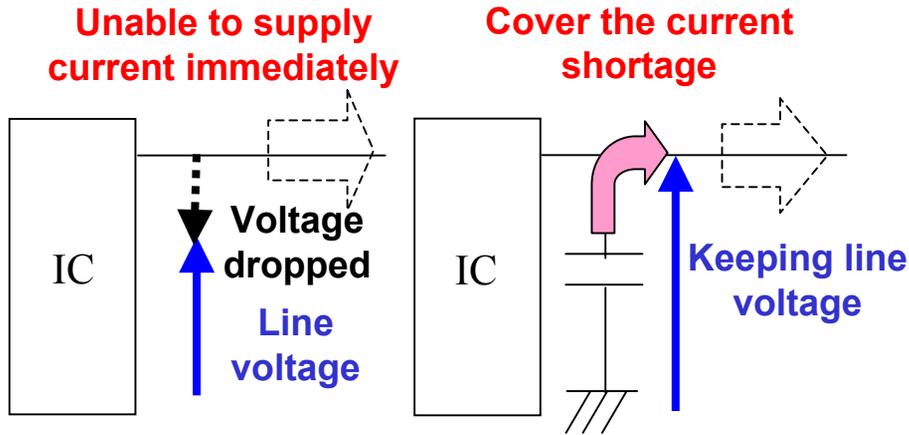


Effects of output capacitor

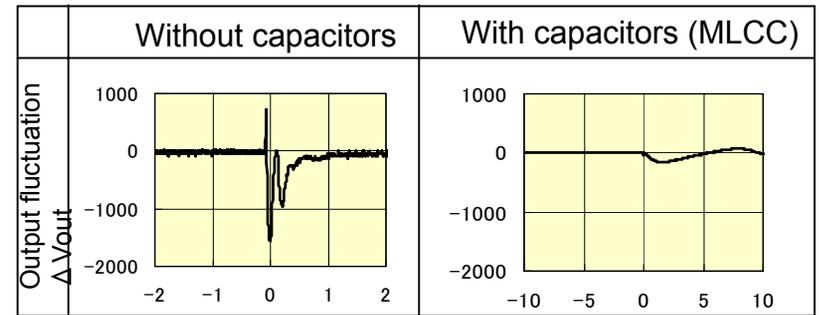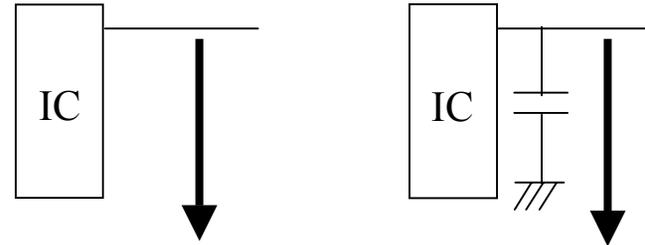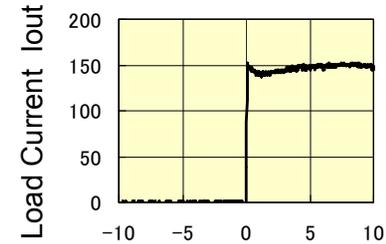Measuring the voltage fluctuation when load change is occurred with/without output capacitor.



Output voltage is stabilized as output capacitor is connected.

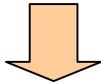Supply current to control voltage fluctuation for rapid load change





Same as the function of Backup Capacitor
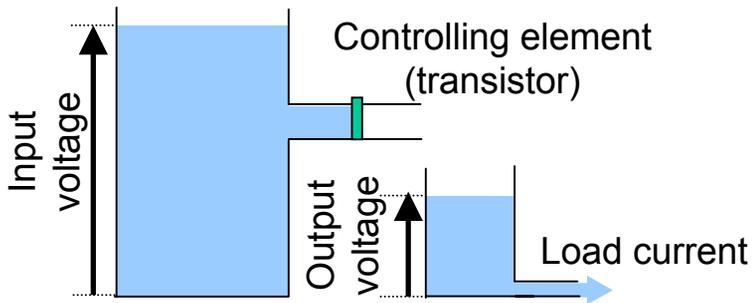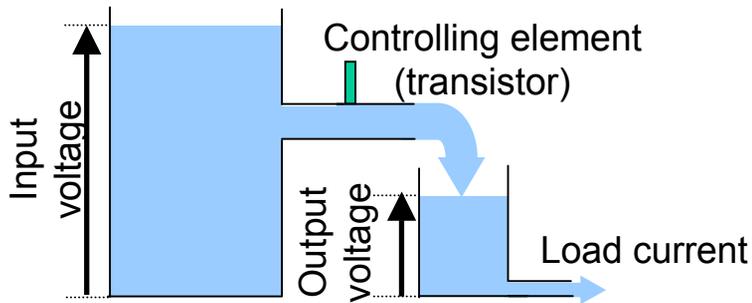
# Step-Down Converter

Circuit operation (water gate model)

Producing output voltage by lowering input voltage with transistor



Transistor for switching power supply has only ON or OFF signal.

Switching operation

Controlling output voltage by switching

Turn-on cycle → Constant

Time to be ON → Changes


→ PWM method

Turn-on cycle → Changes


Time to be ON → Constant

→ PFM method

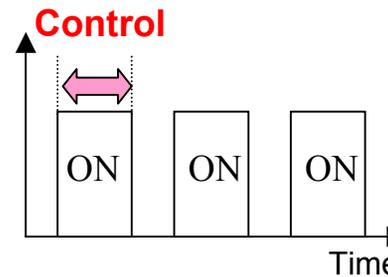Turn-on cycle of the switch → Switching frequency




PWM

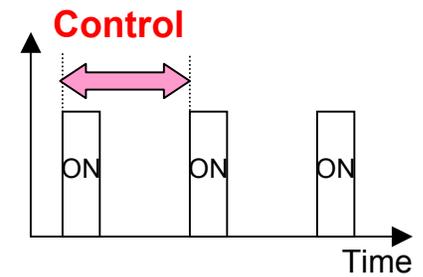


PFM

# Step-Down Converter

## Circuit structure

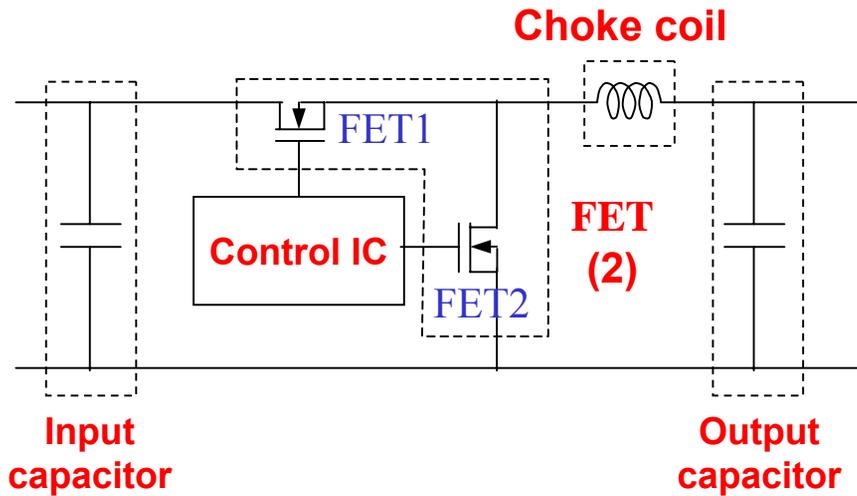


## Input side current

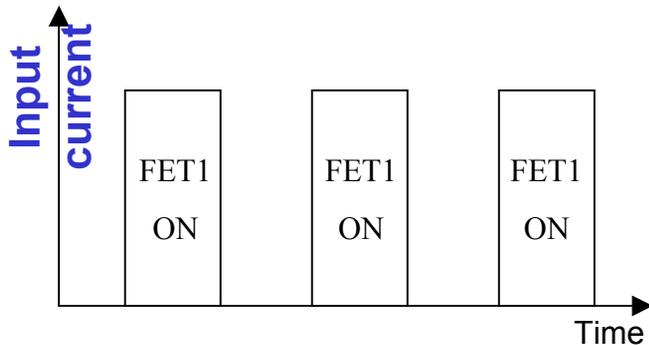

Large amount of alternating current (ripple current) flows.

## Operation of input capacitor

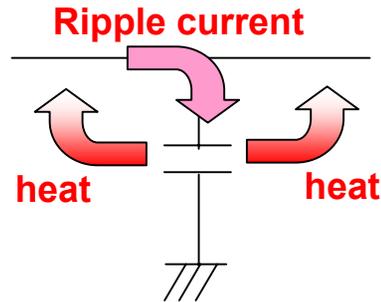


Ripple current flows into input capacitor.

Heat generated by ESR

## Necessary characteristics of input capacitor

High tolerance for ripple current

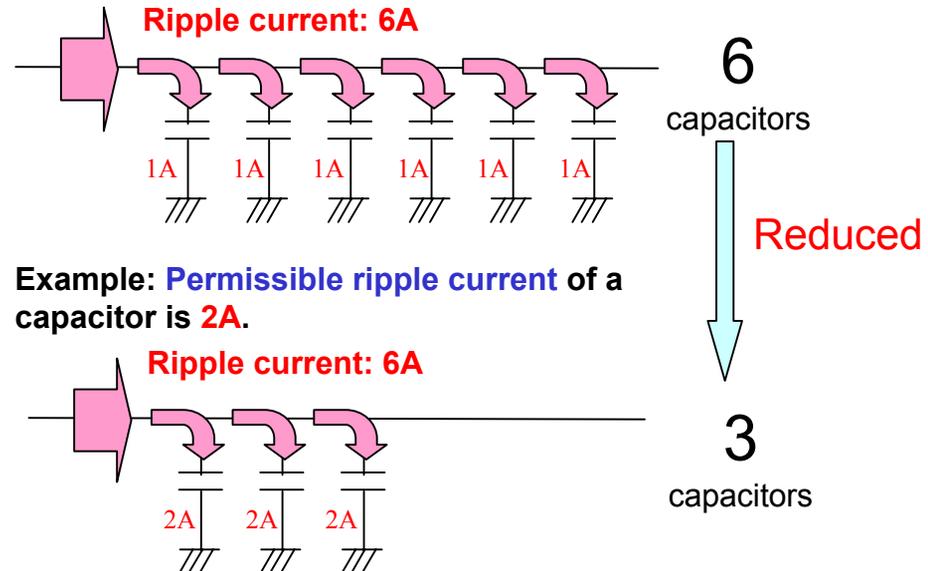
Example: Permissible ripple current of a capacitor is 1A.



Example: Permissible ripple current of a capacitor is 2A.

# Step-Down Converter

Output side operation

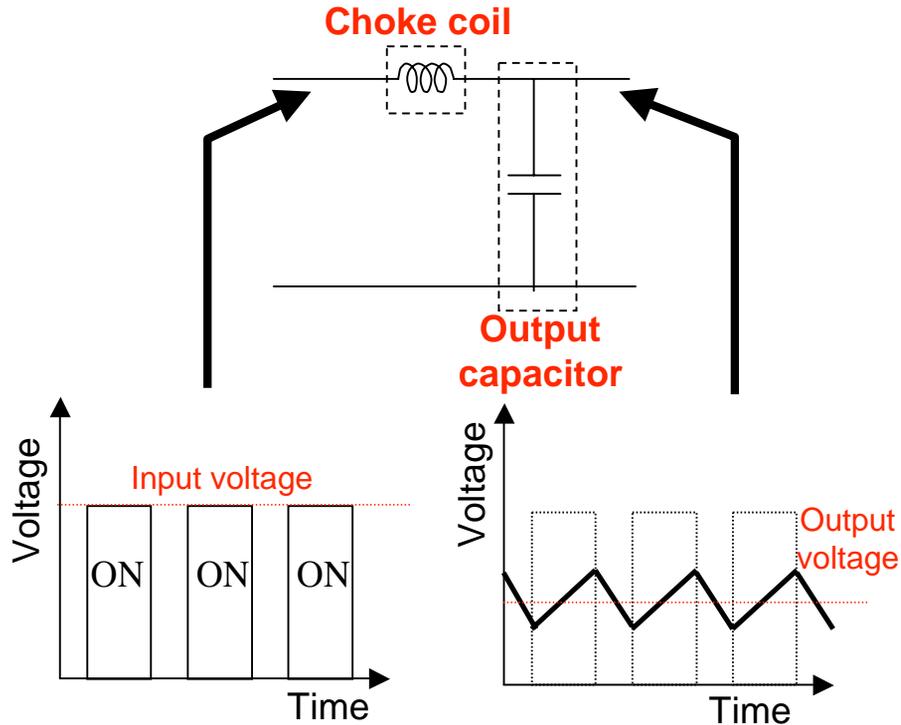

Input voltage is controlled by an on-off switching.

It is smoothed with a choke coil and an output capacitor.




**Ripple voltage is included.**

Points of output voltage to remember

Keeping higher voltage than **the lowest operating voltage** of load IC.


Ripple voltage

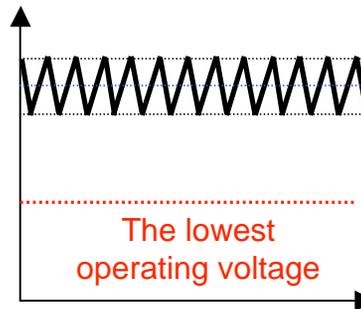

**Rated output voltage**

Keep the band of ripple voltage within the rated value.

Rapid load voltage fluctuation

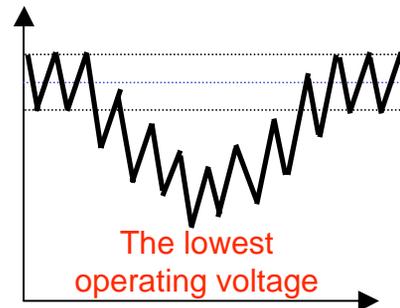


**Rated output voltage**

Control voltage drop by rapid load voltage fluctuation

# Step-Down Converter

Factor for determining voltage drop by rapid load voltage fluctuation

Operation at rapid load change

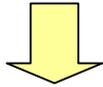

Same as Backup Capacitor

Necessary characteristics for capacitor when rapid load fluctuation occurred


**High capacitance**

→ Supply capacitor of high electronic charge

**Low ESR**

→ Reducing voltage drop when supplying electronic charge

High Value MLCC

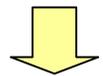

Suitable

Factor for determining ripple voltage

Repeating an on-off switching signal




Charge and discharge are repeated with output capacitor.



Voltage is fluctuated by current flowing in and out.




Ripple voltage

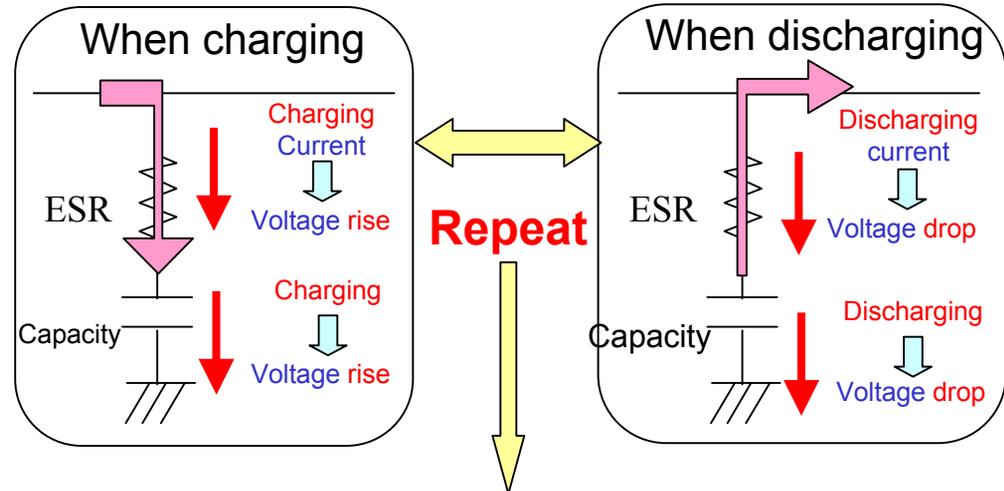

**High capacitance and low ESR**  
reduce ripple voltage.

# Charge Pump (Boost)

Operation of charge pump (image)

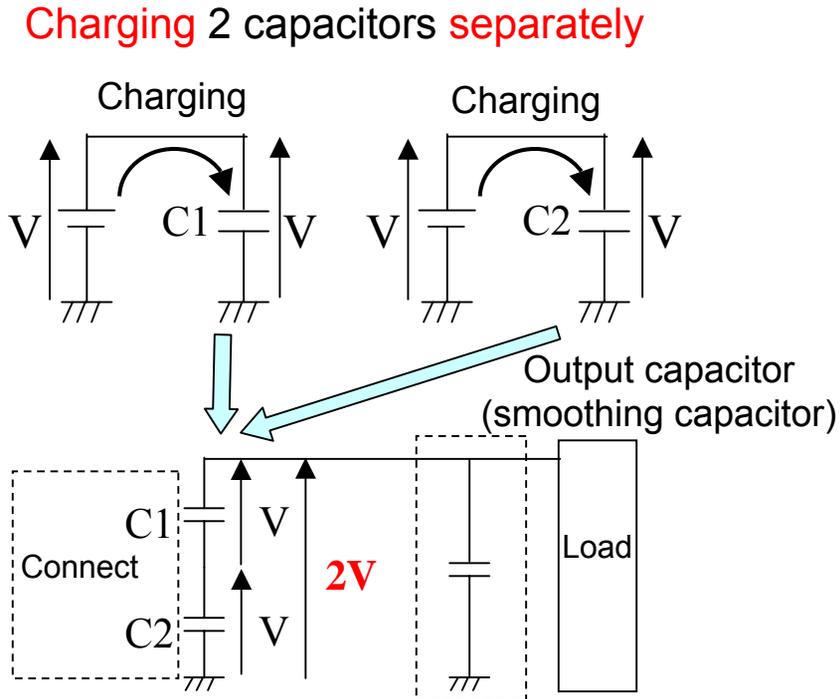


Connecting charged capacitors

Output double amount of voltage than input

Smoothing with output capacitor (Switching)

Output voltage is determined by the number of capacitors connected. (integral multiple)

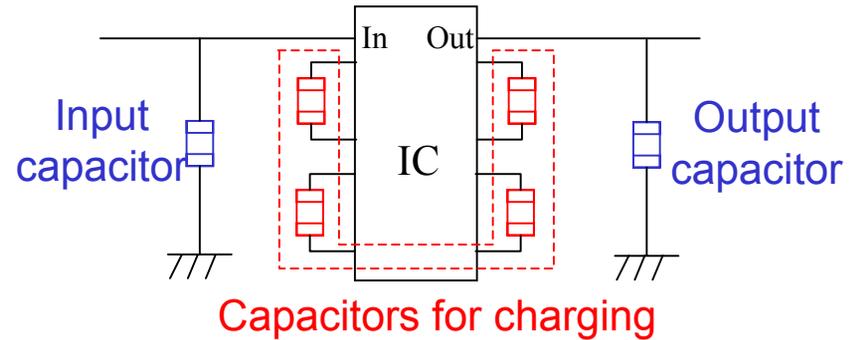Circuitry of charge pump (example: double boost)



Required characteristics of capacitor


Charging capacitor and output capacitor  
→ Lowering voltage fluctuation occurred by charging/discharging

Backup Capacitor  
Same as step-down output capacitor

**High capacitance and low ESR are required.**
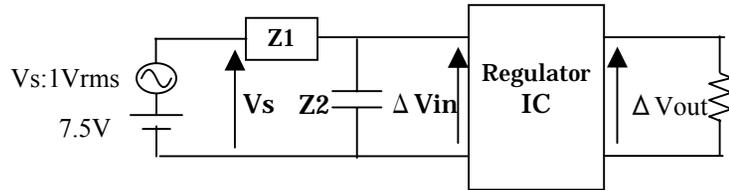
# Summary Comparison of Various Input Capacitors

Measuring the noise absorption and the output voltage fluctuation by adding sine wave on input line



IC used: NJM78L05(JRC)



Capacitor used: MLCC X5R 1uF 10v, Ta1uF, A11uF

$$\Delta V_{in} = \frac{Z_2}{Z_1 + Z_2} V_s \quad (Z_1: \text{Line impedance})$$

Capacitor (Z2) has low impedance.


→ Effect of noise suppression: large

Constant IC input voltage

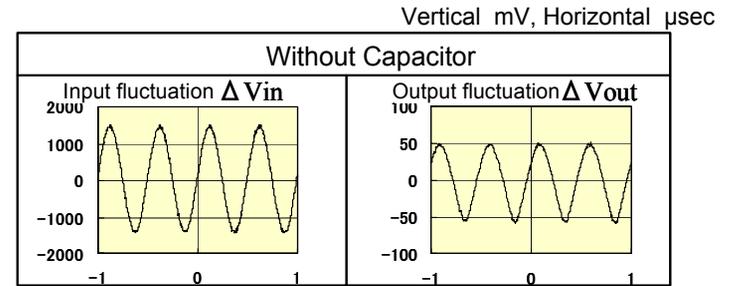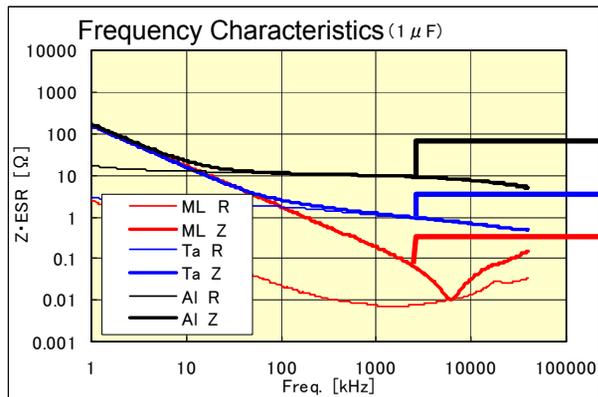


Input fluctuation of 1Vrms → Output fluctuation of 35Vrms

Input capacitor inserted

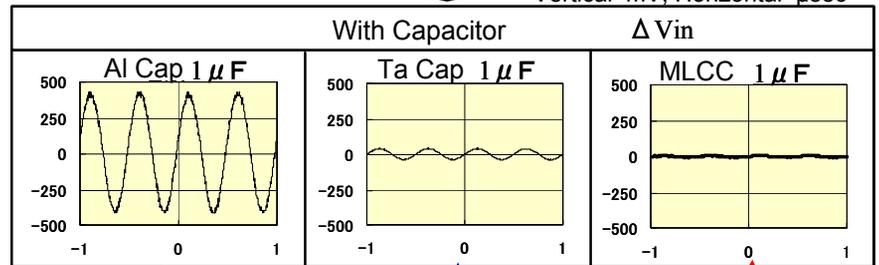

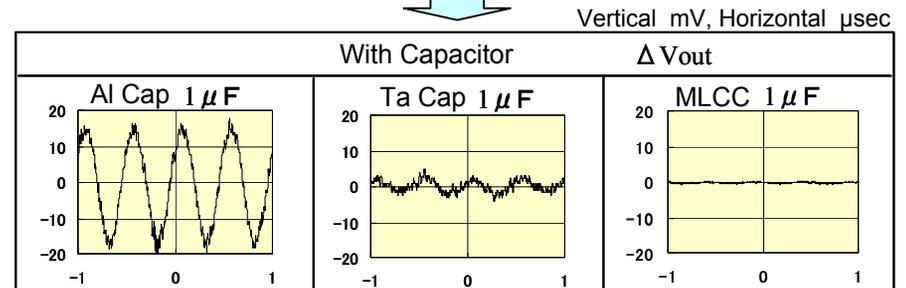MLCC is excellent in noise suppression (low impedance).






Output fluctuation becomes smaller as IC input voltage stays constant.

MLCC has lower impedance than that of Ta for a wide range of frequency.

MLCC is suitable for input capacitor.

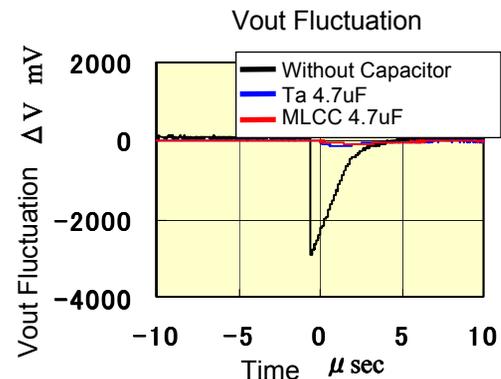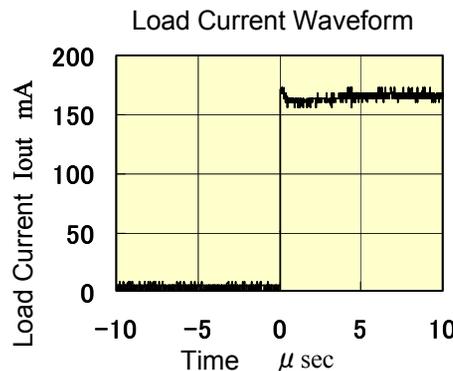
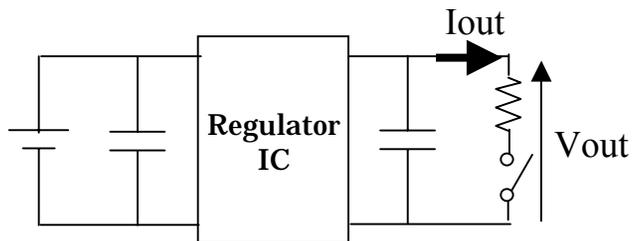
# Summary Operation Analysis of Output Capacitor

Observation of output voltage fluctuation



Waveform observation:  $I_{out}$ ,  $V_{out}$   
(Observing by the type of output capacitors)

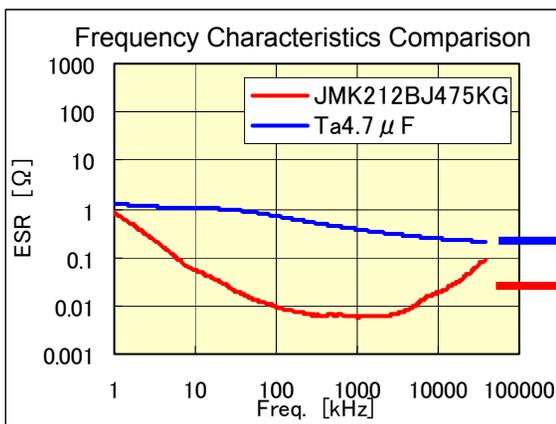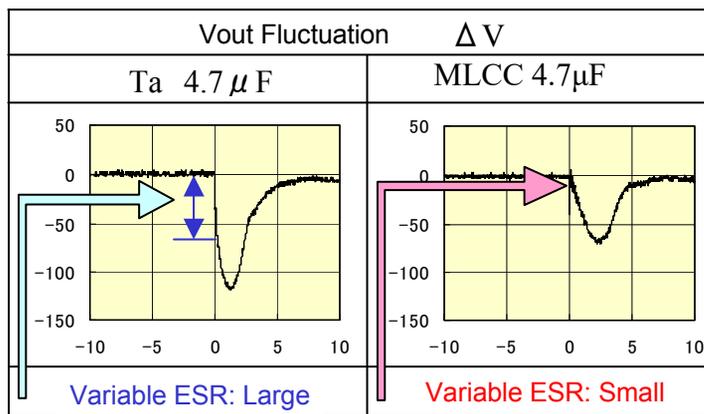IC used: R1112N331B (Ricoh)  
Input Cap: MLCC 4.7 $\mu$ F X5R 10V  
Input V: 5V  
Switching frequency: 100Hz  
Load current: 150mA



ESR: Large

ESR: Small

Vertical mV, Horizontal  $\mu$ sec

Using output capacitor with low ESR reduces the output voltage drop when load fluctuation occurred.

*MLCC with low ESR is well-suitable for output capacitor.*

# Development Method Direction for ML Lineups and Proposals

## Market demand

### Circuit segment

Digital circuit

Analog circuit

Amplifier  
Arithmetic  
Oscillation  
Modem  
Digital  
Power supply

Logic  
High frequency  
Power supply  
Audio  
Others

### Capacitor application segment

Focusing on impedance and ESR characteristics

Decoupling

Backup

Smoothing

High pressure

Filter  
Coupling

Time constant,  
Resonance

Focusing on the stability of real capacitance, temperature and bias

### Required performance

It is for circuit noise suppression and often used in digital circuits.  
**Low Impedance, Low ESR**  
MLCC with Y5V characteristic and 0.1-10uF is best suited

It may also be used for a circuit with large load change (CPU), stability of power line and protection of IC.  
**Low ESR, Low ESL, Low Impedance**  
MLCC with characteristics of Y5V, X5R, X7R and 0.1-10uF is best suited.

It is for in/output of power supply circuit and more used as the miniaturization of equipment.  
**Real capacitance, Low ESR, Low ESL, Low Impedance**  
**Rated Voltage and Reliability**  
MLCC with characteristics of X5R, X7R and 1- tens of uF is best suited.

It is for amplifier, arithmetic, modem and filter circuits.  
**Stability of capacitance temperature and bias is important.**  
Temperature compensating dielectric type MLCC is best suited.  
(CFCAP, TC type multilayer)